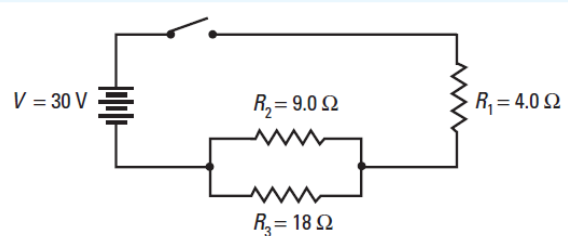


Analyzing Complex Circuits



Resistors in Parallel

Find the equivalent resistance of the entire circuit shown in the diagram, as well as the current through, and the potential difference across, each load.



$$\frac{1}{R_A} = \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_A} = \frac{1}{9.0 \Omega} + \frac{1}{18 \Omega}$$

$$\frac{1}{R_A} = \frac{2}{18 \Omega} + \frac{1}{18 \Omega}$$


$$\frac{1}{R_A} = \frac{3}{18 \Omega}$$

$$\frac{1}{R_A} = \frac{1}{6.0 \Omega}$$

$$R_A = 6.0 \Omega$$

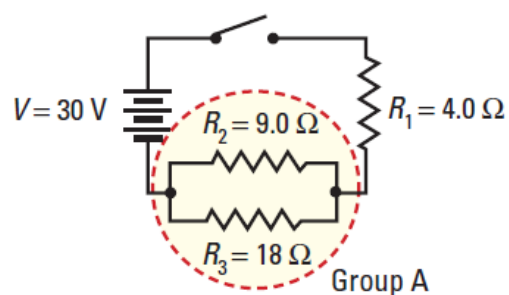
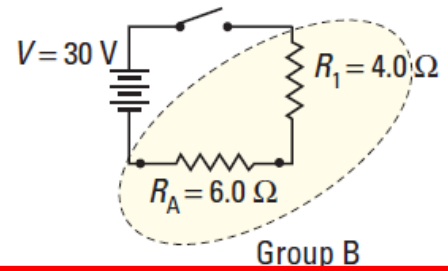
$$R_B = R_A + R_1$$
$$R_B = 4.0 \, \Omega + 6.0 \, \Omega$$
$$R_B = 10 \, \Omega$$



$$V = IR$$

$$I_S = \frac{V_S}{R_{\text{eq}}}$$

$$I_S = \frac{30 \, \text{V}}{10 \, \Omega}$$

$$I_S = 3.0 \, \text{A}$$

