

#24)

Strategy

Apply Ohm's law.

Use the expression for the electric current to solve for the charge and use the fact that A·s is equivalent to C.

Calculations

$$V = IR$$

Substitute first

$$12 \text{ V} = I(5.8 \ \Omega)$$

$$12 \text{ V} \cdot \frac{1}{5.8 \ \Omega} = (5.8 \text{ A}) \frac{I}{12 \ \Omega}$$

$$I = \frac{12 \text{ V}}{5.8 \ \Omega}$$

$$I = 2.07 \text{ A}$$

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(2.07 \text{ A})(480 \text{ s})$$

$$= \frac{Q}{480 \text{ s}}(480 \text{ s})$$

$$Q = (2.07 \text{ A})(480 \text{ s})$$

$$Q = 990 \text{ C}$$

#25)

Strategy

Use the expression for the potential difference.

The amount of work done is equal to the potential energy.

Solve for the charge.

Calculations

$$V = \frac{\Delta E_Q}{Q}$$

$$W = \Delta E_Q$$

$$W = 3.35 \times 10^5 \text{ J}$$

Substitute first

$$(120 \text{ V})Q = \frac{3.35 \times 10^5 \text{ J}}{\cancel{Q}} \cdot \cancel{Q}$$

$$\frac{(120 \text{ V})Q}{120 \text{ V}} = \frac{3.35 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = \frac{3.35 \times 10^5 \text{ J}}{120 \text{ V}}$$

Solve for Q first

$$VQ = \frac{\Delta E_Q}{\cancel{Q}} \cdot \cancel{Q}$$

$$\frac{VQ}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{3.35 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = 2.80 \times 10^3 \text{ C}$$

$1 \frac{\text{J}}{\text{V}}$ is equivalent to 1 C, thus

#25)-continued

Use the expression for the electric current to solve for the current.

Substitute and divide.

$1 \frac{\text{C}}{\text{s}}$ is equivalent to 1 A, thus

Apply Ohm's law.

$$I = \frac{Q}{\Delta t} \quad \text{.....}$$

$$I = \frac{2.80 \times 10^3 \text{ C}}{270 \text{ s}}$$

$$I = 10.3 \text{ A}$$

$$V = IR$$

Substitute first

$$120 \text{ V} = (10.3 \text{ A})R$$

$$120 \text{ V} \cdot \frac{1}{10.3 \text{ A}} = (10.3 \text{ A}) \frac{R}{10.3 \text{ A}}$$

$$R = \frac{120 \text{ V}}{10.3 \text{ A}}$$

$$R = 11.6 \Omega$$

Solve for R first

$$V = IR$$

$$V \cdot \frac{1}{I} = \frac{R}{I}$$

$$R = \frac{120 \text{ V}}{10.3 \text{ A}}$$

$$R = 11.6 \Omega$$

The resistance is 11.6Ω .

#26)

Strategy

Use the expression for the potential difference.

The amount of work done is equal to the potential energy.

Solve for the charge.

$\frac{1}{\text{V}}$ is equivalent to 1 C, thus

Apply Ohm's law.

Calculations

$$V = \frac{\Delta E_Q}{Q}$$

$$W = \Delta E_Q$$

$$\Delta E_Q = 4.32 \times 10^5 \text{ J}$$

Substitute first

$$(240 \text{ V})Q = \frac{4.32 \times 10^5 \text{ J}}{\text{V}} \cdot \text{V}$$

$$\frac{(240 \text{ V})Q}{240 \text{ V}} = \frac{4.32 \times 10^5 \text{ J}}{240 \text{ V}}$$

$$Q = \frac{4.32 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = 1800 \text{ C}$$

$$V = \frac{I}{R}$$

Substitute first

$$240 \text{ V} = I(60.0 \Omega)$$

$$240 \text{ V} \cdot \frac{1}{60.0 \Omega} = (60.0 \text{ A}) \frac{I}{12 \Omega}$$

$$I = \frac{240 \text{ V}}{60.0 \Omega}$$

$$I = 4.00 \text{ A}$$

#26) - continued

Use the expression for the electric current to obtain the time.

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(4.00 \text{ A})\Delta t = \frac{1800 \text{ C}}{\Delta t}\Delta t$$

$$\Delta t = \frac{1800 \text{ C}}{4.00 \text{ A}}$$

$1 \frac{\text{C}}{\text{A}}$ is equivalent to 1 s.

$$\Delta t = 450 \text{ s}$$

It would take 450 s or $450 \text{ s} \frac{1 \text{ min}}{60 \text{ s}} = 7.50 \text{ min}$ for the battery to do the amount of work.